

IA-32 Architecture

Computer Organization and Assembly Languages


Yung-Yu Chuang

2005/09/29

with slides by Kip Irvine and Keith Van Rhein

Virtual machines

Abstractions for computers

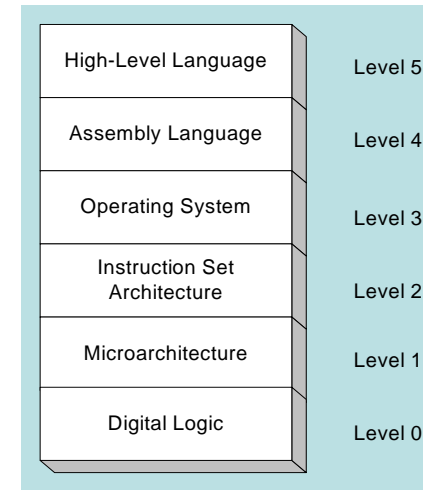


NOT

- Inverts (reverses) a boolean value
- Truth table for Boolean NOT operator:

X	$\neg X$
F	T
T	F

Digital gate diagram for NOT:

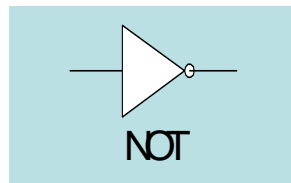


AND

- Truth if both are true
- Truth table for Boolean AND operator:

X	Y	$X \wedge Y$
F	F	F
F	T	F
T	F	F
T	T	T

Digital gate diagram for AND:

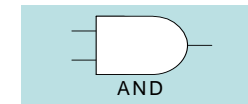


OR



- True if either is true
- Truth table for Boolean OR operator:

X	Y	$X \vee Y$
F	F	F
F	T	T
T	F	T
T	T	T

Digital gate diagram for OR:

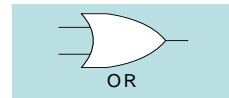

Truth tables



- A Boolean function has one or more Boolean inputs, and returns a single Boolean output.
- A truth table shows all the inputs and outputs of a Boolean function

Example: $\neg X \vee Y$


X	$\neg X$	Y	$\neg X \vee Y$
F	T	F	T
F	T	T	T
T	F	F	F
T	F	T	T

All possible 2-input Boolean functions



0 0 0 0	0		1 0 0 0	NOR	
0 0 0 1	AND		1 0 0 1	XNOR	
0 0 1 0	xy'		1 0 1 0	y'	
0 0 1 1	x		1 0 1 1	$x + y'$	
0 1 0 0	$x'y$		1 1 0 0	x'	
0 1 0 1	y		1 1 0 1	$x' + y$	
0 1 1 0	XOR		1 1 1 0	NAND	
0 1 1 1	OR		1 1 1 1	1	

Truth tables

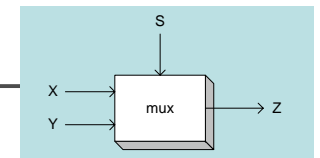


Two-input multiplexer


- Example: $(Y \wedge S) \vee (X \wedge \neg S)$

X	Y	S	$Y \wedge S$	$\neg S$	$X \wedge \neg S$	$(Y \wedge S) \vee (X \wedge \neg S)$
F	F	F	F	T	F	F
F	T	F	F	T	F	F
T	F	F	F	T	T	T
T	T	F	F	T	T	T
F	F	T	F	F	F	F
F	T	T	T	F	F	T
T	F	T	F	F	F	F
T	T	T	T	F	F	T


4-multiplexer

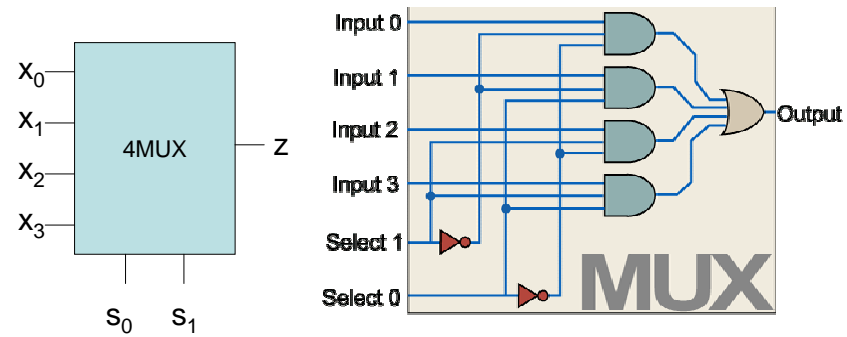


4-multiplexer

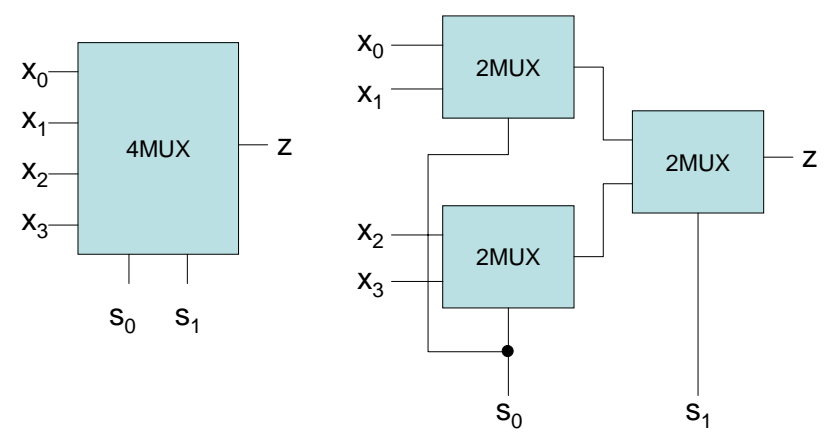

Comparator

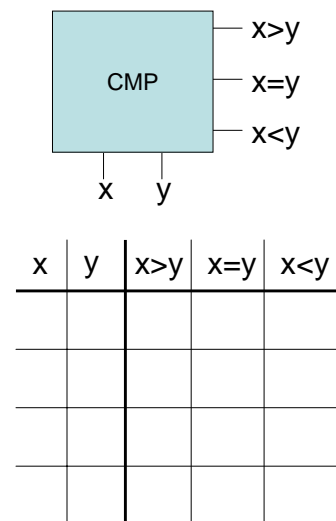


8-bit comparator

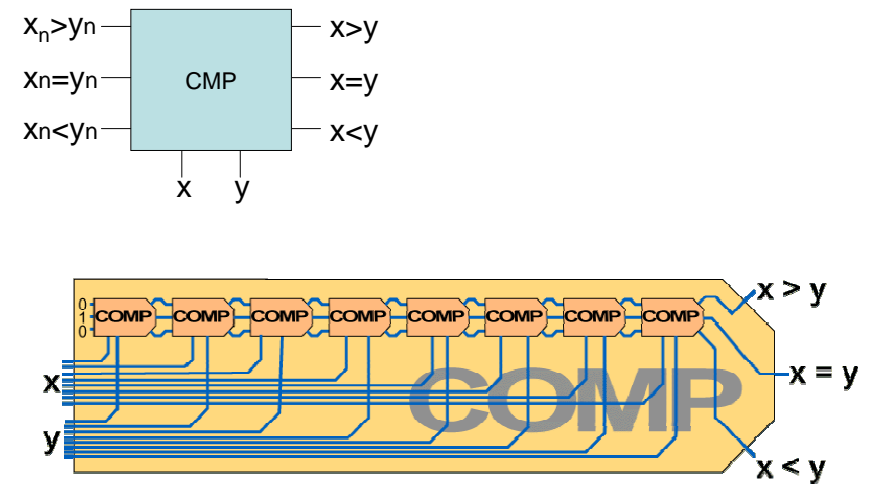


1-bit half adder



x	y	s	c

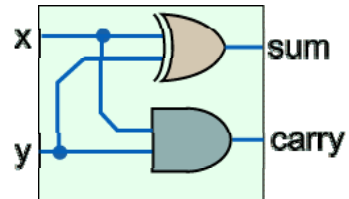


1-bit full adder

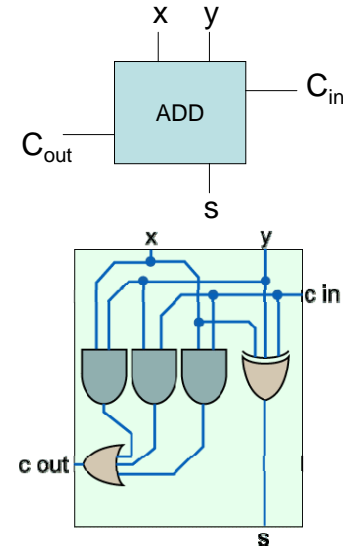


x	y	C _{in}	C _{out}	s


8-bit adder

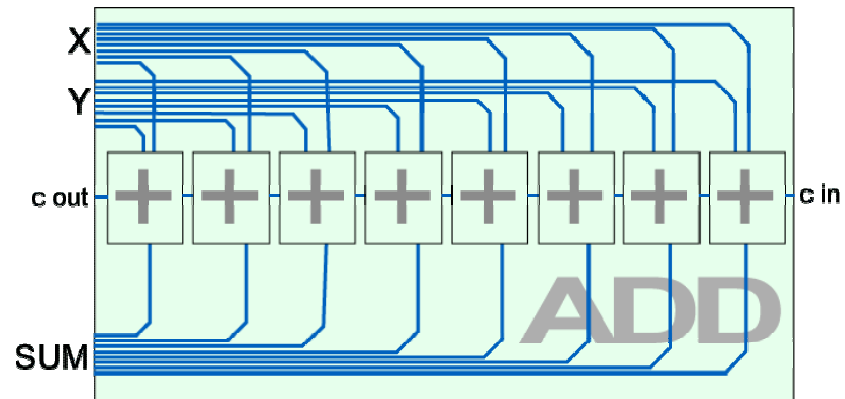

Registers and counters

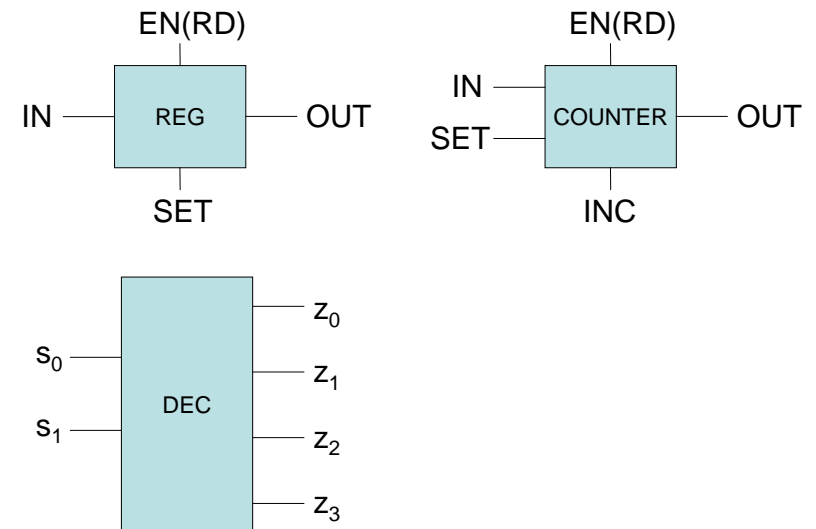

Memory

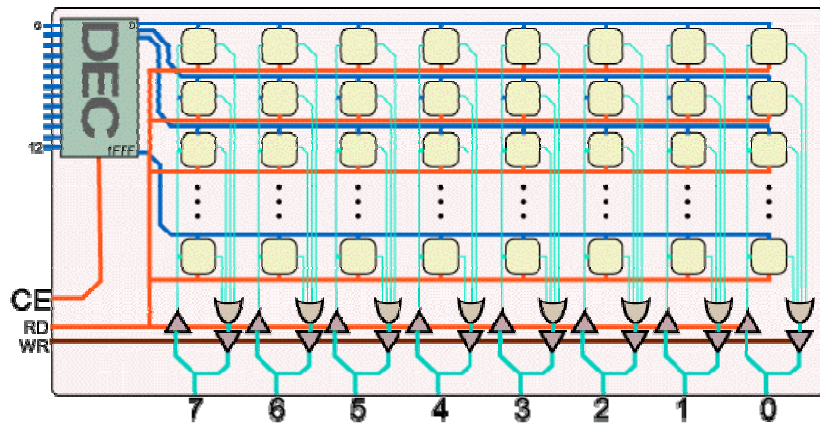


8K 8-bit memory

Microcomputer concept


Basic microcomputer design

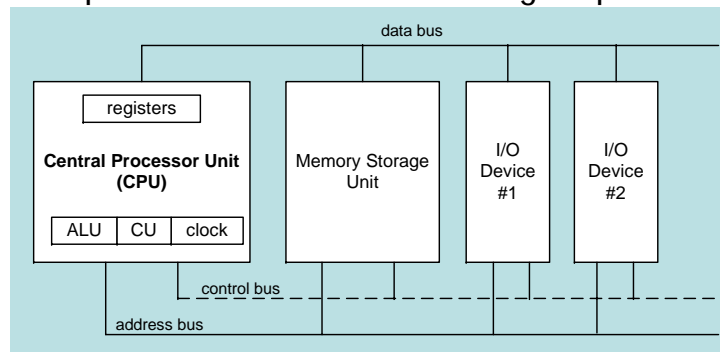- clock synchronizes CPU operations
- control unit (CU) coordinates sequence of execution steps
- ALU performs arithmetic and logic operations




Basic microcomputer design

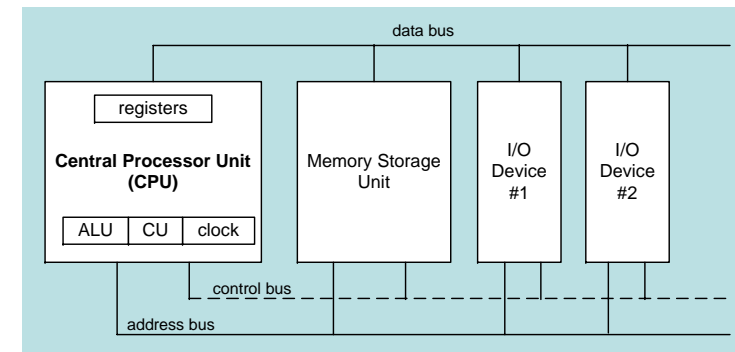- The memory storage unit holds instructions and data for a running program
- A bus is a group of wires that transfer data from one part to another (data, address, control)




Clock

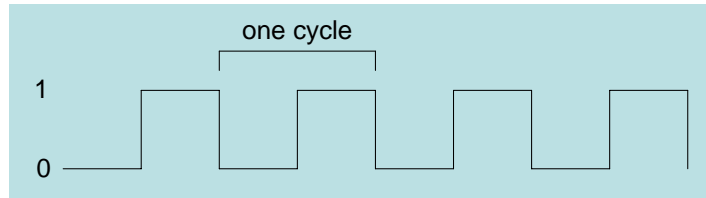- synchronizes all CPU and BUS operations
- machine (clock) cycle measures time of a single operation
- clock is used to trigger events




- Basic unit of time, 1GHz \rightarrow clock cycle = 1ns
- A instruction could take multiple cycles to complete, e.g. multiply in 8088 takes 50 cycles

Instruction execution cycle

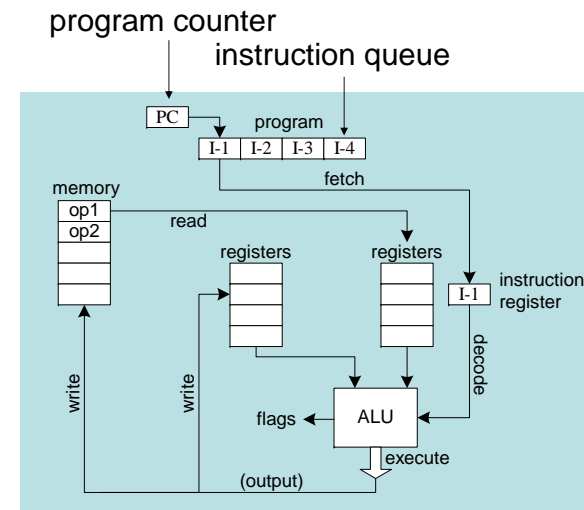


- Fetch
- Decode
- Fetch operands
- Execute
- Store output

A simple microcomputer

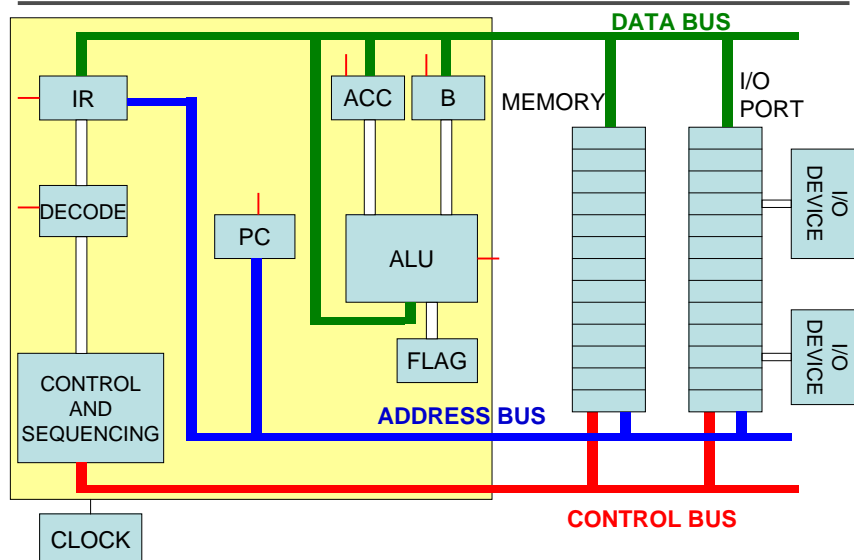

Instruction set

OPCODE	MNEMONIC	OPCODE	MNEMONIC
0	NOP	A	CMP
1	LDA	B	JG
2	STA	C	JE
3	ADD	D	JL
4	SUB		
5	IN		
6	OUT		
7	JMP		
8	JN		
9	HLT		

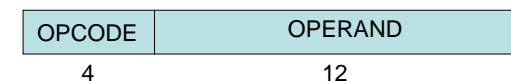


Control bus



- A series of control signals to control all components such as registers and ALU
- Control signal for load ACC:
 $SET_{ACC}=1$, others=0

Control and sequencing unit

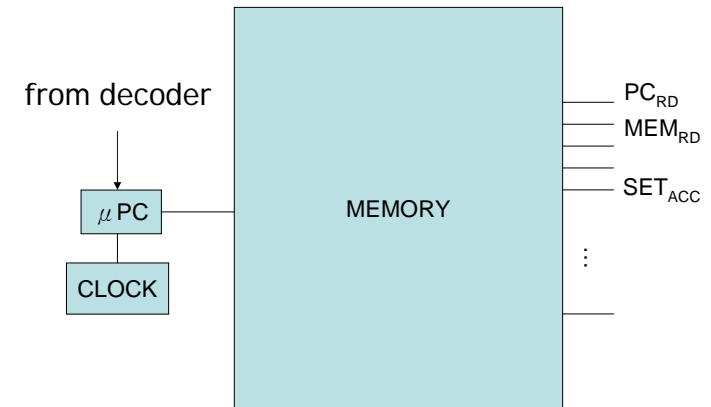

Control and sequencing unit



		PC _{RD}	MEM _{RD}	MEM _{WT}	IR _{SET}
fetch	0000	1	0	0	0	0....
	0001	0	1	0	0	
	0002	0	0	0	1	
decode	0003	4-bit IR RD				
	0004	DECODER RD, μ PC SET				
exec	0005					
fetch						
decode						
	000B					

Decoder

